

# Digital IC - Summary

Thomas Debelle

- Introduction
  - Transistor switch model
- Logic Circuits
  - Regeneration of the level
  - Capacitance
    - \* Effective fan-out
    - \* Signal in reality
  - Pass gate logic
    - \* Level restoration
- Circuit Timing / Dynamic Logic
  - Latch/Register Implementation
  - Sequencing, pipelining revisited
    - \* Clock skew
  - Dynamic logic
    - \* Charge coupling
    - \* Cascading dynamic logic
    - \* Clocked CMOS or  $C^2$ MOS
    - \* Conclusion
- 5 - Production Test
  - Introduction: what's the problem
    - \* Ad hoc versus structured test
  - Structured test
    - \* Structural testing
  - Design for testability
  - Summary
- 6 - Low Energy Design
  - Fight the battle at all levels
  - (micro)Architectural choices
    - \* Signal Gating
    - \* Dilemma
  - The plumber's manual
    - \* Power gating
    - \* Variable Threshold CMOS
    - \* Long-Le transistors
    - \* Stacking effect
    - \* Standby vector
  - Sizing and multiple supply voltages
    - \* Energy Delay Sensitivity
    - \* Circuit analysis of Energy and Delay
    - \* Example Chain of inverter
  - Ultra low voltage design examples
    - \* TG: Building pipelines

## Introduction

One of the main thing about this class is finding how to optimize the ratio of  $Op/s/W = Op/J$ . We want to enhance this ratio. Less and less foundry have smaller and smaller technology. We want to reduce it both for *plugged* and *battery* device. Either we don't have the requirements to pull out or the space to store the energy.

This class is all about Gate and transistor. Low level is king.

## Transistor switch model

We can model a switch (MOSFET) with an ideal switch and a resistor :

 


Figure 1: Switch

By the transistor scaling, short channel are behaving differently due to the **velocity saturation**. The relation becomes linear and not quadratic like it used to be.

- case 1 :  $V_{min} = V_{DS} \rightarrow$  Linear region

$$I_{DSAT} = \mu C_{ox} \frac{W}{L} \left( (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

- case 2 :  $V_{min} = V_{GS} - V_T \rightarrow$  (Channel) Saturation

$$I_{DSAT} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

- case 3 :  $V_{min} = V_{DSAT} \rightarrow$  Velocity Saturation

$$I_{DSAT} = \mu C_{ox} \frac{W}{L} \left( (V_{GS} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right) (1 + \lambda V_{DS})$$

Figure 2: Equations

## Logic Circuits

The swing here is equal to  $V_{dd}$  so we have a high noise margin. It is not a **ratioed** logic so we can't use tricks to minimize mismatch by taking advantage of ratios. We only have 1 resistor on so low output impedance but the input is the gate of MOS so we have a high input impedance. There is no static power consumption since no direct path from Vdd to ground. That's nice :)

In the dynamic model we need to add an output cap  $C_L$ . The load cap is simply the sum of all capacitance at the output node. Transition time is determined by the charging of this cap by a resistor. The sizing impacts the dynamic behavior of the gate.

Ideally we want  $V_M$  to be at the middle of the other nominal voltage. We call the region in between the *undefined region*.

## Regeneration of the level

With using this type of gate we have some regeneration level, it will amplify the signal and so we won't have undefined level and we will have the signal that will reach one defined state. If we have no regeneration, we will

 


Figure 3: Regions

 


Figure 4: The static model

 


Figure 5: Switching threshold

 


Figure 6: NAND gate regeneration

reach meta-stability. We have to meet some conditions :

- The transient or undefined region in the VTC should have a gain  $|dV_{out}/dV_{in}|$  larger than 1
- In the “legal” or defined regions the VTC gain should be smaller than 1 in absolute value
- The boundary between the defined and undefined regions are  $V_{IH}$  and  $V_{IL}$  where the gain = -1

We need gain or the signal will be lost.

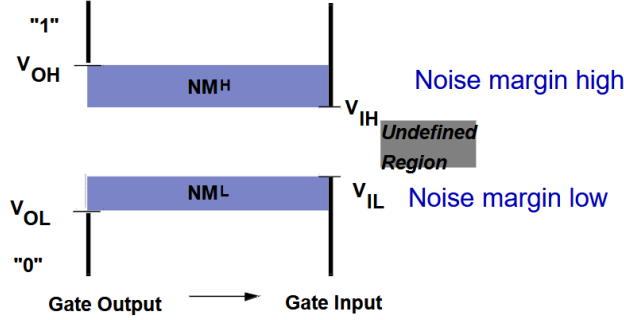


Figure 7: Noise margin

We have 3 different types of noise :

1. Inductive coupling
2. Capacitive coupling
3. Power and ground noise

The noise margin in CMOS is rather high which is a good thing seeing the low output impedance.

$$\begin{aligned}
 I_n(V_{GS} = V_M) + I_p(V_{GS} = V_M - V_{DD}) &= 0 \\
 k_n V_{DSATn} (V_M - V_{Tn} - \frac{V_{DSATn}}{2}) + k_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2}) &= 0 \\
 \text{Solving for } V_M \text{ yields} \\
 V_M = \frac{(V_{Tn} + \frac{V_{DSATn}}{2}) + r(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2})}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} \\
 \text{The ratio } (W/L)_p / (W/L)_n \text{ to set a certain } V_M \text{ is given by} \\
 \frac{(W/L)_p}{(W/L)_n} = \frac{k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k_p V_{DSATp} (V_{DD} - V_M + V_{Tp} - V_{DSATp}/2)} \text{ (both TOR in velocity saturation!)}
 \end{aligned}$$

Figure 8: Switching threshold for INV

We see that the ratio of PMOS and NMOS determine the  $V_M$  voltages.

## Capacitance

We know that the delay of a switch is  $t_{phl} = f(R_{on}C_L) = \ln(1/2)R_{on}C_L = \ln(1/2)(R_{eqn} + R_{eqp})/2 \cdot C_L$ . We are still observing some glitches when we switch on and off. This **isn't** due to the miller effect. This **overshoot** is due to the gate drain capacitor.

This is due to charges and sudden and “infinite” steep step at the input which will create an extra unwanted voltage. Thankfully the input isn't as steep in reality and so the effect is less severe but still noticeable. We call it the *digital miller effect*:

$$t_d = \frac{C_{total} \cdot (\Delta V + V_{DD}/2)}{I_{max}} = \frac{(C + C_L)}{I_{max}} \left( \frac{C}{C + C_L} V_{DD} + \frac{V_{DD}}{2} \right) = \frac{(3C + C_L) \cdot V_{DD}}{2I_{max}}$$

So it is like the cap becomes 3 times larger (similar to the miller effect) but in reality we are closer to 2 since we never have a perfect step at the input.

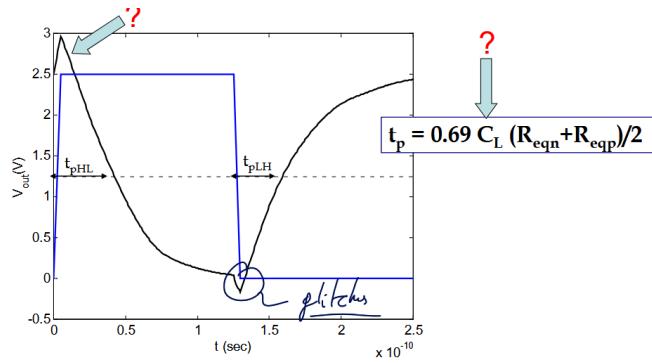


Figure 9: Glitches and Delay


 


Figure 10: Explanation of the overshoot

- We analyse the influence of  $C_{gd34}$  on the delay of Inverter  $I_1$
- $C_{gd34}$  is loading node B, but
  - $C_{gd34}$  is first charged  $\frac{+}{-} \parallel \frac{+}{-}$
  - when node B is switching node C is at ground,
- Charge required to bring node at 0 and discharge  $C_{gd34}$  is  $C_{gd34} \cdot V_{DD}$
- When node C finally switches
  - $C_{gd34}$  is charged  $\frac{+}{-} \parallel \frac{+}{-}$
  - requiring another charge  $C_{gd34} \cdot V_{DD}$

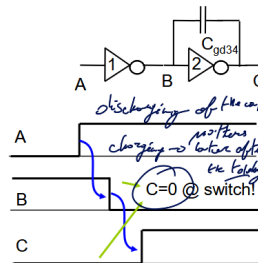

Conclusion: "Recharging"  $C_{gd34}$  requires a charge of  $2 \cdot C_{gd34} V_{DD}$ , but only half of it is exchanged during the switching of  $I_1$   
 $\Rightarrow C_{gd34}$  is seen only "once" in the delay of  $I_1$

Figure 11: Loading issue

We can move those  $C_{gd}$  to the inside and see it as an impact on  $C_L$ . Again we can reuse the theory of DDP with the intrinsic and extrinsic load where  $C_L = C_{int} + C_{ext}$  :

$$t_p = 0.69R_{eq}(C_{int} + C_{ext}) = 0.69R_{eq}C_{int} \left(1 + \frac{C_{ext}}{C_{int}}\right) = t_{p0} \left(1 + \frac{C_{ext}}{C_{int}}\right)$$

So the sizing can help up to a certain point where we have an *irreducible* delay.

### Effective fan-out

The input  $C_g$  and intrinsic cap are always proportional to the sizing :  $C_{int} = \gamma C_g$  where  $\gamma$  is a technological constant. Same goes for the extrinsic load  $C$  where it is the input  $C$  of the next inverter proportional to the sizing  $C_{ext} = f C_g$ . So we can summarize the delay  $t_p$  by :

$$t_p = t_{p0} \left(1 + \frac{f}{\gamma}\right)$$

The delay depends on the ratio between its external load capacitance and its input capacitance, the ratio is called the *effective fan-out*.

The newly introduced  $\gamma$  is not valid for dynamic logic or more exotic technologies. If this  $\gamma = 1$  then it means that  $C_{int} = C_{in}$ . It is an acceptable approximation in standard CMOS logic.

$$t_p = kR_w C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / \gamma)$$

$$\begin{aligned} C_{int} &= \gamma C_{gin} \text{ with } \gamma \approx 1 \\ f &= C_L / C_{gin} - \text{effective fanout} \\ R &= R_{unit} / W ; C_{int} = W C_{unit} \\ t_{p0} &= 0.69 R_{unit} C_{unit} \\ R_{unit} &\sim 1 / V_{DD} \end{aligned}$$

Figure 12: The golden formula

For the ring oscillator where we assume equal size  $f = 1$  is independent of the size. In real technology we see only a weak dependency of timing on sizing.

### Signal in reality

We know that we can't have infinitely steep signal and even worse, a too slow rise and fall time could lead to metastability issues ! We could also have some actual short circuit for a brief amount of time leading to waste of energy. So in most of design software we will leave some headroom to avoid possible short-circuit and we will flag it with *max transition violation*.

**Note on sizing** When we see the  $a$  or  $b$  next to a transistor it is its *relative sizing* compared to a classic  $\frac{W_{min}}{L_{min}}$ . For complex gate and due to the various sizing we can have, we will transform a little bit our formula :

$$t_p = t_{p0} \left(p + \frac{gf}{\gamma}\right) = t_{p0} d$$

- $f$  : electrical effort
- $g$  : logical effort
  - due to the fact a logical gate is always slower than an inverter with equal current drive. Ratio of input cap to the cap of an inverter that delivers equal current.
- $p$  : ratio of intrinsic delay of the gate to the intrinsic delay of an inverter
- $d$  : gate delay
  - relative to the intrinsic delay of the reference inverter

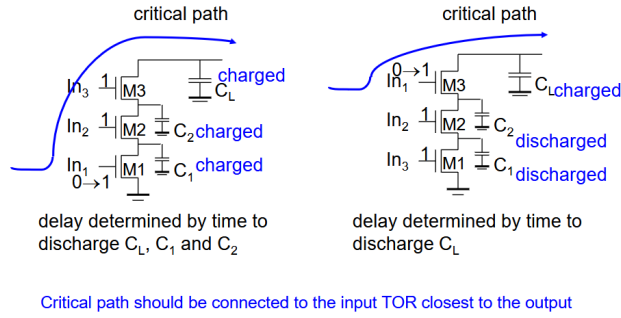


Figure 13: Critical path & Charging

## Pass gate logic

Another approach than PUN and PDN as seen previously is the pass gate logic where we will not only use the gate but also the source of a transistor to create some gate.

 


Figure 14: Pass gate logic

This technique uses less transistors. But the NMOS isn't a really good pull up transistor. It won't give a nice and crisp high voltage but rather a voltage with a  $\Delta V = V_{T_{loss}}$ . So to keep this signal crisp and nice we are obligated to add an INV to output a valid signal. This goes in the same idea as the *regeneration of the signal* logic.

So cascading of passes tor logic isn't a smart choice since the signal will rapidly deprecate.

 


Figure 15: Static analysis

## Level restoration

So we need to do what we call *level restoration*.

It is compatible with the full swing and the static power consumption is gone. But we need a bleeder which will increases capacitance at node X and takes away the pull down current. Leads to speed degradation and needs proper sizing.

**Transmission gate** We can add a PMOS to the switch to create a **transmission gate**. This requires another transistor but also a complementary signal is needed so this will result in extra cost.



 


Figure 16: Level restorer

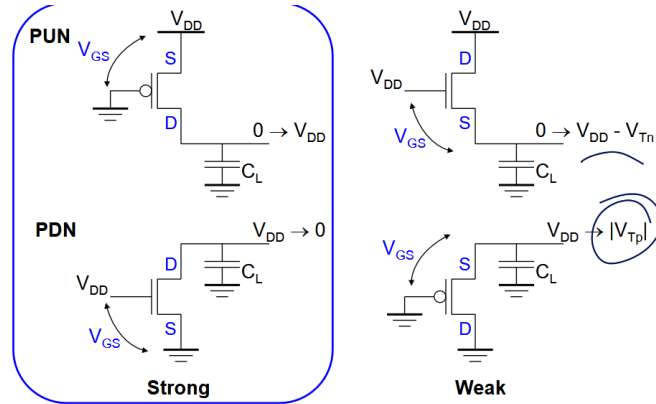


Figure 17: Threshold drops generalized

## Circuit Timing / Dynamic Logic

### Latch/Register Implementation

We know that having 2 INV back to back could lead to meta-stability so how can we reliably store data ? We want to remember the data *no triggering* but also sample and so stop looping the data *triggering*. In the second approach we simply *overpower the feedback loop* due to the asymmetry of the INV and so the input D will be more important than the output of the small INV (**David-Goliath latch**). Or we can cut the loop like in the second example.

 


Figure 18: Latches

Specifications	Positive Latch	Register
Storage ?	store when clock is low	Stores on rising edge
Transparent ?	Yes when clock is high	No

For latches we can either go for positive or negative latches and a register is simply two latch back to back. We can do latches using MUX for example.

The second option is more preferable because it will have less load on the CLK which reduce the energy waste. But we need to remember we have to *regenerate* the signal since we will have a  $V_{Tloss}$ .

The latch is pretty similar to the idea we have seen with pass gate. Here we can see again the bleeder on top and NMOS on the bottom which forms a basic INV.

**NEED TO READ THIS PART CAREFULLY**

 


Figure 19: Mux-Based latch : Transmission Gate vs Switch


 


Figure 20: David Goliath

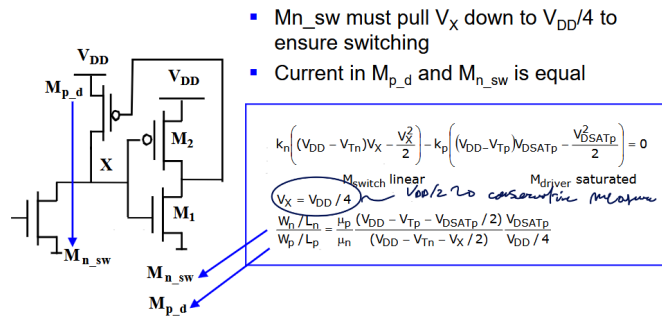

This is a worst case approach. In practice the bleeder will already be "weakened" because at  $V_X = V_{DD}/4$ , the inverter has already begun to switch off.

Figure 21: Sizing of the latch

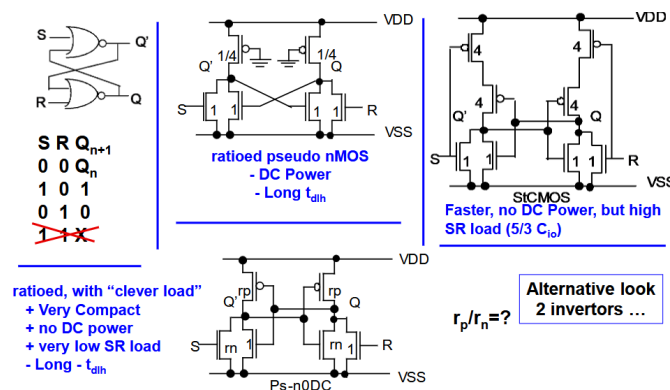


Figure 22: NOR-NOR latch

 


Figure 23: NAND-NAND latch


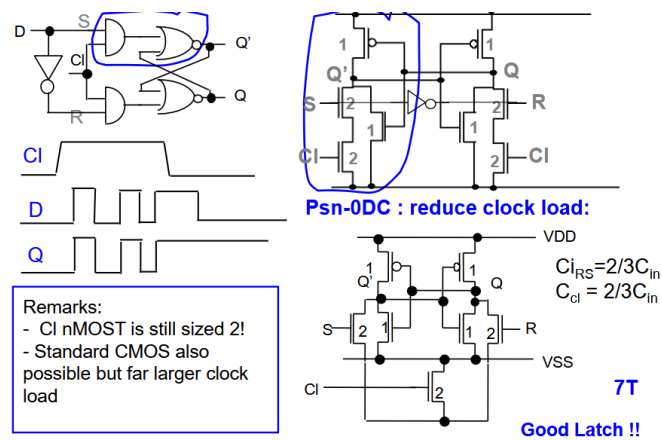


Figure 24: Transparent (n-)latch

## Finite State Machines - Controllers

 

## Datapath


 
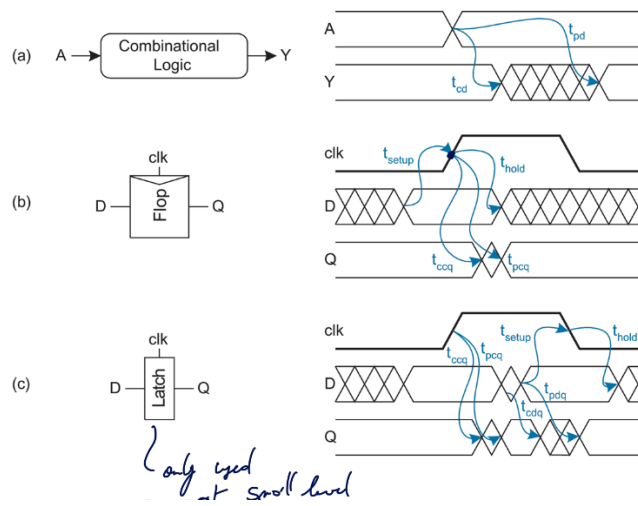
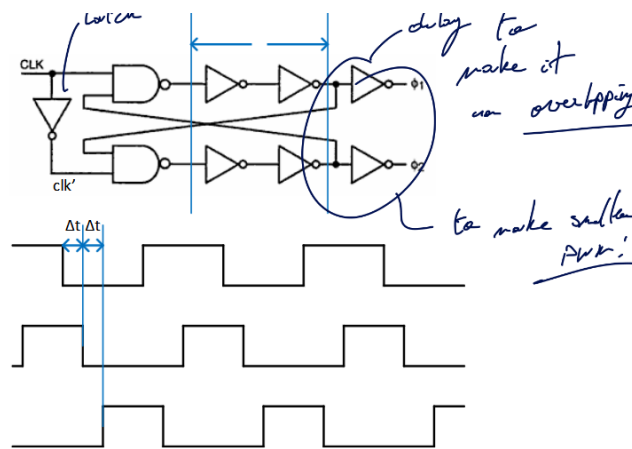


Figure 25: Registers in the system

 

$$T_c > t_{pd} + \underbrace{t_{pcq} + t_{setup}}_{\text{sequencing overhead}} \quad t_{cd} + t_{ccq} > t_{hold}$$

 


Figure 29: latches, max. delay

$$t_{cd} + t_{ccq} + t_{nonoverlap} > t_{hold}$$

In the registers logic, we set the clock speed based on the slowest logic section. But in latch logic, we can do some **time borrowing** technique to take some time from the next cycle. We can't do this if we loop the data over in which case we will have some overlap of processing data.

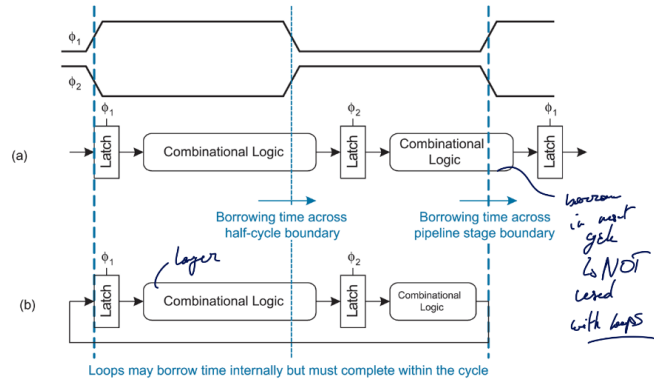


Figure 30: Time borrowing technique

To compute the maximum allowed borrow time is based also on the setup time :

$$t_{borrow} < T_c/2 - (t_{setup} + t_{non\_overlap})$$

### Clock skew

It is the fact the clock will have to propagate to gates and it can take less or more time depending on the travel distance. It is a deterministic phenomena. The statistical one is jitter which is not taken into account in this course.

We can use a **clock tree** structure to balance the clock and to make sure that the path taken for all the components is of the same length. It is not always feasible. It is also influenced by interconnect properties.

If we do latch logic the timing is not impacted by  $t_{skew}$  since the *signal has the whole transparent phase to arrive*.

$$t_{pd} = t_{pd1} + t_{pd2} < T_c - 2 \cdot t_{pdq}$$

And for time borrowing we get :

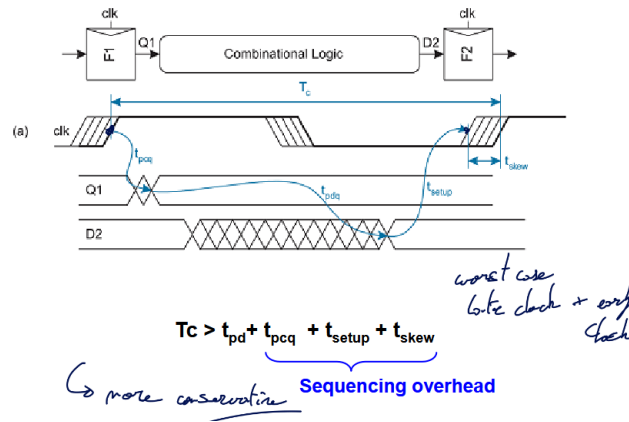


Figure 31: Clock skew effect

$$t_{borrow} < T_c/2 - (t_{setup} + t_{non\_overlap} + t_{skew})$$

For the validity we have :

$$\text{FF: } t_{cd} + t_{ccq} - t_{skew} > t_{hold} \quad \text{Latch: } t_{cd} + t_{ccq} + t_{non\_overlap} - t_{skew} > t_{hold}$$

	Sequencing overhead ( $T_c - t_{pd}$ )	Minimum logic delay ( $t_{cd}$ )	Time borrowing ( $t_{borrow}$ )
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0 (doesn't exist)
Two-Phase Transparent Latches	$2 \cdot t_{pdq}$	$t_{hold} - t_{ccq} - t_{non\_overlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{non\_overlap} + t_{skew})$

## Dynamic logic

The idea behind *dynamic logic* is to charge and discharge a node that has a high impedance. While in static logic the output is either connected to VDD or GND via a low resistive path.

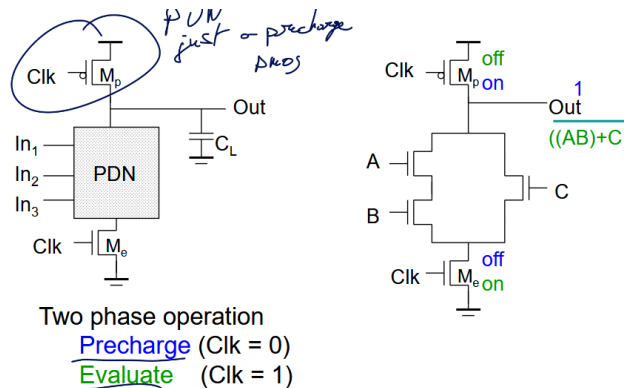


Figure 32: Example of a dynamic logic circuit

We use the low CLK to charge and then evaluate when it is high. So if we discharge by mistake, we will have to wait the next clock cycle. There is 0 or 1 transition during evaluation. We can keep the node high before or after evaluation.

We only need to create a PDN which represent the function we are trying to produce only  $N + 2$  (so less transistor compared to static logic  $2 \cdot N$ ). We have full swing outputs. No need to ratio size and we have a faster switching speed since the output and input line has less capacitance. Less logical effort.

But we have a higher power dissipation than static logic. The line is always active and for a continuous set of 0 we need to load and discharge all the time the cap. We have a low noise margin since the PDN will start working as

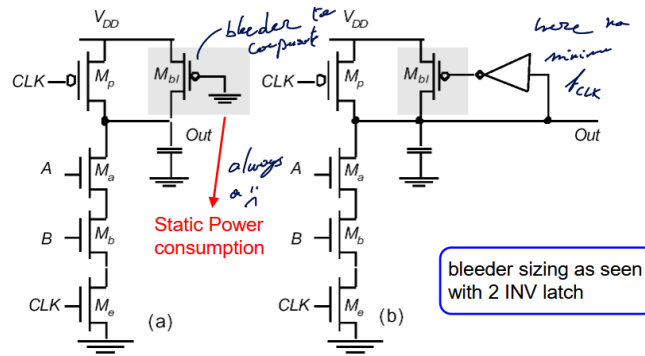


Figure 33: Bleeder and Level restorer

One way to avoid this is to precharge the internal nodes. But we need more transistor, more energy and it will increase the  $C$  making the circuit slower.

### Charge coupling

It is also pretty sensitive to charge coupling. So any wire-to-wire crosstalk can be disastrous. There is also the backgate coupling or output to input coupling that can be problematic. We should also avoid clock feedthrough and overshoot.

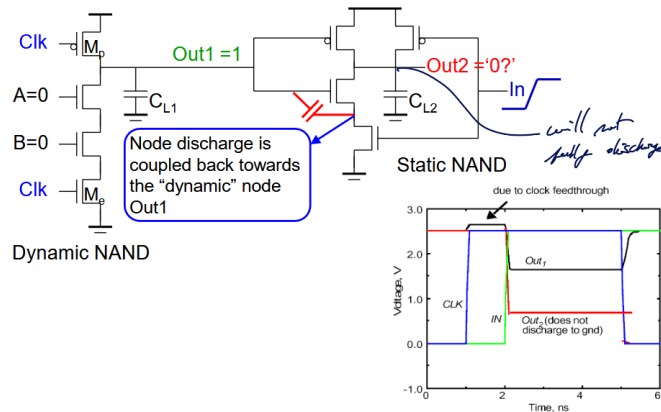


Figure 34: Output to Input coupling

 


Figure 35: Clock feedthrough

Danger: charge injection in the substrate. Charge can be collected by HiZ node or lead to latch-up.

**Latch-up** It is an annoying phenomena where the substrate of MOS transistors has a parasitic thyristor junction we can cause latch-up and put the transistor in an unwanted state. To reset, we need to cut-off the power of the

circuit and start again. (More info: Weste N., e.a. "Principles of CMOS VLSI design – a systems perspective. Second Edition", Addison Wesley, 1993)

 


Figure 36: Latch-up

## Cascading dynamic logic

 


Figure 37: Cascading dynamic logic

The finite propagation delay from in to out1 will cause a partial discharge at out2 which can again makes the output 2 invalid resulting in unwanted behavior.

**Domino logic** To avoid this we can add an inverted between the two stages. So any transition from charged to discharge or keep will result into a valid state. The static inverter is like a buffer and we need some extra logic to restore the correct output.

 


Figure 38: Domino logic

We can add some skew to the inverter since the only critical transition is the  $1 \rightarrow 0$  one. We reduce the impact impedance. Only non-inverting logic can be implemented ! So we either need to do some logic transformation (not always possible) or use **dual rail domino**.

**Dual rail domino logic** We need to construct 2 PDN one where we do  $F(A, B, C) = (A \& B) | C$  or any function and then its NOT version  $\overline{F(A, B, C)}$  using *De Morgan's* theorem. So only one branch will switch on and only one side will make a transition. But it comes at the expense of area and continuous switching no matter the result.

**Alternative to cascade of dynamic logic** A good alternative is to switch between PDN and PUN networks so the  $0 \rightarrow 1$  transition are allowed at inputs of PDN and  $1 \rightarrow 0$  transitions are allowed at inputs of PUN.

**Dynamic edge triggered register** We use a capacitor as a storage source that we need to refresh. We can't simply halt the clock. It is sensitive to  $0 \rightarrow 0$  and  $1 \rightarrow 1$  transition and to clock overlap. But we have good performance



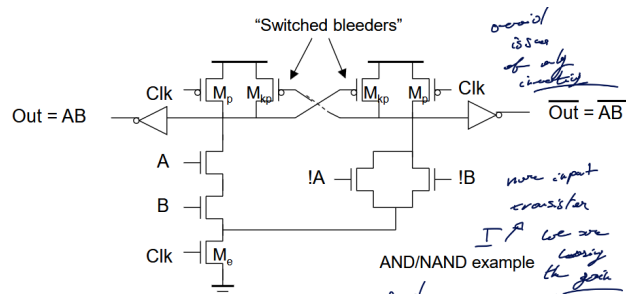


Figure 39: Dual rail domino logic - using switched bleeders

 


Figure 40: Alternative

 


Figure 41: Dynamic edge triggered register

## Clocked CMOS or $C^2$ MOS

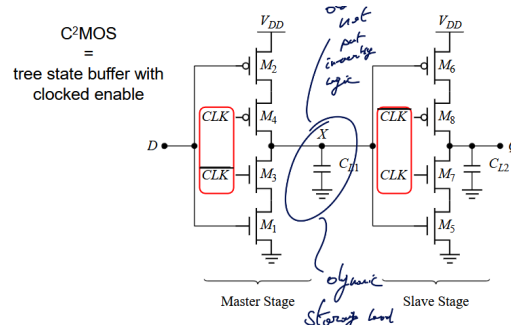


Figure 42:  $C^2$ MOS

Now it is no longer sensitive to clock overlap just need a fast enough rise and fall times.

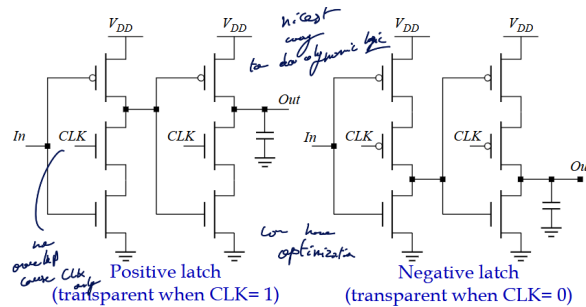


Figure 43: TSPC logic

**True Single Phase Clock (TSPC) logic** Here we only have 1 clock phase so easy to distribute the clock and no overlap by construction. At first when  $CLK = 1$  we have like 2 inverters and so the latch is transparent. But when  $CLK = 0$ , the charge can't be pulled down and if we have  $In = 0$ , the output won't change since the inverter will stop the propagation of that value.

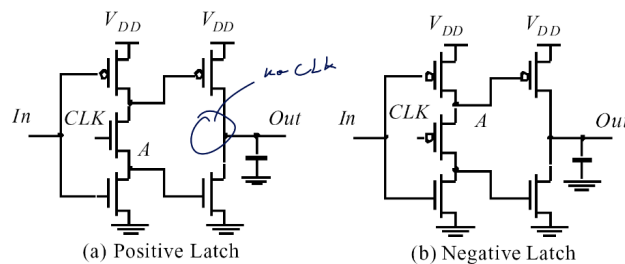


Figure 44: TSPC simplification - split output

It has less TOR and clock load but the split outputs don't have full swing. We have less drive, less VDD scaling possibility.

## Conclusion

- Due to its high impedance nature, design of dynamic circuits is tricky and requires extreme care at the circuit level.
- Hard to automate in a synthesis – P&R flow based on static CMOS standard cells
- Power consumption of dynamic logic is usually higher.
- Nothing is as easy as standard CMOS...

## 5 - Production Test

We cannot build a working chip that is not testable, no one would buy our chip if we can't demonstrate that a specific die is working. This is why we need production test, to demonstrate that each of our sample is working as expected.

### Introduction: what's the problem

Let's dive in.

#### Ad hoc versus structured test

We have two type of cost:

- Non recurring cost: development cost, engineer salary
- Recurring cost: testing the chip, the time it takes us, the reduced throughput

We need to increase the *observability* and *controlability* but adding more pins is expensive for IC, so we need to use a **scanning technique** where we load in a buffer we can observe all the data. We can also add more controlability by using muxes that are driven by a test mode signal. This a **ad hoc method** of testing.

But we don't always have this available. We don't always know how everything works.

#### Structured test

We could just enumerate all possible state, But with  $n$  inputs and  $m$  states, we have  $2^{m+n}$  tests, which quickly explode and we can't just test all possible combinations.

#### Structural testing

It is based on the fault models and knowledge of the circuit structure. We can predict or check for specific defect and use the **Automatic Test Pattern Generation (ATPG)**

#### Design for testability

TODO

#### Summary

TODO

## 6 - Low Energy Design

We have some fundamental equations related to power and energy:

$$E_{dyn} = QV_{dd} = CV_{dd}^2 \quad P_{stat} = V_{dd}I_{leak} \quad E_{stat} = V_{dd}I_{leak}t_d$$

### Fight the battle at all levels

$$P = \alpha CV_{dd}^2 f_{clk} + I_{subth} V_{dd}$$

The most simple idea is to:

- Kill activity  $\alpha$
- Reduce cap  $C$
- Reduce  $V_{dd}$
- Clock slower  $f_{clk}$
- Less leakage  $I_{subth}$

Activity factor is a software dependent value and analysis tools can use statistic to estimate the switching probability but it isn't perfect.

In this course we focus on circuit design and architecture. So we can play with  $V_{DD}$ , use more or less parallelism, do some signal and clock gating, ...

All this level of abstraction can sometimes obfuscate the fact that two circuits can have different power performance. It can be hard to locate and to monitor it with the complexity of modern tools.

## (micro)Architectural choices

Due to combination logic and the fact that we may go through multiple level of gates, we can have some glitches: so an unwanted, unnecessary transition that is synonym of wasted energy.

Typically, this glitch issue is present in Ripple Carry Adder (RC Adder). To avoid it, we can adopt a **tree structure** to balance the delay path and so to avoid unwanted transition. We can think of the *Log adder*.

The **logic depth** is the source of this glitch and so pipelining will help it.

## Signal Gating

To avoid such glitches or overall unwanted transition, we can do signal gating and avoid signal propagation. But we need more circuitry and power, so it is a trade-off and optimization problem.

Signal gating is only interesant if we toggle the gate less often than the signal that we block or let pass. Even better is sharing a control signal between multiple part of the circuit. We usually uses clock, data buses, ...

**Guarded evaluation** One implementation of this idea is **guarded evaluation** where we will trigger the evaluation only if we know we want its result next clock cycle.

**Precomputation** Here we check the if condition earlier and avoid propagating useless inputs.

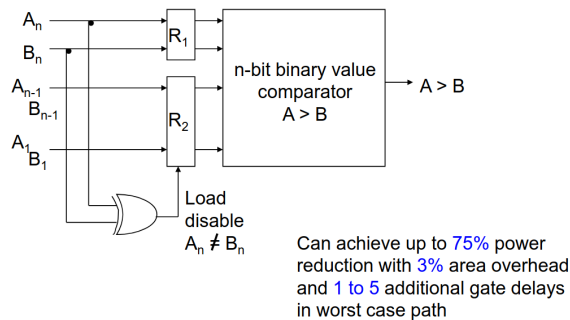


Figure 45: Precomputation

**Clock gating** Can be done automatically and efficiently but introduce *skew* and *testability problems*.

## Dilemma

The biggest dilemma here is the trade-off between more hardware and slower speed which is better for the *dynamic POV*. But more hardware means more leakage which is bad for *static leakage*.

If we lower the supply near  $V_T$  we know that:

$$I_D = I_0 e^{\frac{V_{dd} - V_T}{n k T / q}}$$

So we will still have some current ... We can reduce the supply but we will have lower speed, less difference between  $I_{on}$  and  $I_{off}$  and more sensitive to variation. The speed isn't an issue for many application in reality and luckily enough, products that run at those frequency usually want low energy usage. Win-win situation for once.

But let's not get overwhelmed and keep in mind the actual FoM is *E/op* not who got the smallest supply. In fact, going to low will at some point increase the current consumption at some point.

Hard to quantify the *sign off* and it changes from one netlist to the other quite drastically.

## The plumber's manual

### Power gating

Usually, we want to cut-off the logic that is no longer in use. We will implement the logic in **Low VT** and the switch network in **High VT** because:

- **Low VT**: high leakage but good performance
- **High VT**: low leakage

But when turning off the logic, we still want to keep the results of our previous calculation. For this, we need a **keeper** that needs low leakage.

Also, switching the network on and off is not a good thing and we will have a penalty due to the charging and discharging of the cap  $C_p$  and  $C_n$ .

### Variable Threshold CMOS

$V_T$  isn't fixed as seen in DIAC, we can model it with:

$$V_T = V_{T0} \pm \gamma \left( \sqrt{2|\varphi_F - v_{BS}|} - \sqrt{2|\varphi_F|} \right)$$

So changing  $v_{BS}$  will bias the  $V_T$ . We call this Reverse Body Bias.

### Issues

- $\gamma$  becomes smaller with scaling
  - Need more negative PSS which is costly and not always reliable
- Substrate is a large cap, so pretty slow and costs energy
- $V_T$  has an impact on performance

FDSOI is one solution that is talked about in the next chapter.

**Forward body bias** Used here to increase performance but we can go up to a certain point or we won't reverse the junction properly. It is quite complicated to control and should only be used where performance is absolutely critical.

**Multiple Threshold CMOS** The best thing to do is to mix technologies of CMOS and use sometimes low or high  $V_T$  transistor.

### Long-Le transistors

Another technique is to have longer length of transistor by about 10% compared to the nominal length. They are 10% slower but have **3 times lower leakage**. So whenever we have a path that have some slacks we will replace the transistor by this type of transistor.

One common practice, is to start designing with long Le transistor and then when we want to reach timing, we will reduce its length for the critical path.

Such Le transistors are often more appreciated as they don't require multiple power supply and is more effective.

 


Figure 46: Techniques and their effects

 


Figure 47: Stacking effect

## Stacking effect

If one drain lets water out why not building another one a lil further down the river ?

That's what they thought when introducing this technique or something similar. It can drastically reduce leakage but will gives us less headroom for our design:

We can have some natural stacking (because of the nature of the logic) or *forced stacking* where we will split one NMOS into two parts to reduce leakage.

## Standby vector

One last technique is to use *standby vector* that will force a 1 or 0 in standby mode.

## Sizing and multiple supply voltages

We saw in platforms how minimizing delay and energy is an optimization problem where we need to find the best tradeoff. On top of that, we need to stay between the rail, have a large enough transistor and respect  $V_T$ .

## Energy Delay Sensitivity

To compare various technology or implementation we can take a look at the sensitivity where:

$$S_A = \frac{\partial E / \partial A}{\partial D / \partial A} \Big|_{A=A_0}$$

It is a powerful tool as it indicates the *effectiveness of changes* in design. With this, comes a lot of theory about optimality but one thing that is important here is the **pareto-optimality**.

## Pareto-optimal

the best that can be achieved without disadvantaging at least one metric

So basically, we can reduce one metric without raising another one. The two curves have various sensitivity.

$$\Delta E = S_A \cdot (-\Delta D) + S_B \cdot \Delta D$$

## Circuit analysis of Energy and Delay

When analyzing  $i$  and  $i + 1$  logic gates we can find the delay to be (like in DDP):

$$t_d = \frac{K_d V_{DD}}{(V_{DD} - V_T)^\alpha} \left( \frac{\gamma C_i + C_W + C_{i+1}}{\gamma C_i} \right) = \tau_{nom} : \left( 1 + \frac{C'_{i+1}}{\gamma C_i} \right)$$

$$E_{dyn} = (\gamma C_i + C_W + C_{i+1}) \cdot V_{DD,i}^2 = C_i(\gamma + f'_i) \cdot V_{DD,i}^2$$

Where  $C_i = K_e S_i$ ,  $f'_i = (C_W + C_{i+1})/C_i = S'_{i+1}/S_i$ , giving us:

$$E_i = K_e S_i (V_{DD,i-1}^2 + \gamma V_{DD,i}^2)$$

We can then derivate the sensitivity to sizing:

$\frac{\partial E / \frac{\partial D}{\partial S_i}}{\frac{\partial D}{\partial S_i}} \left  \begin{array}{l} E = \sum_i E_i \\ E_i = K_e S_i (V_{DD,i-1}^2 + \gamma V_{DD,i}^2) \\ \frac{\partial E}{\partial S_i} = \frac{\partial E_i}{\partial S_i} = K_e (V_{DD,i-1}^2 + \gamma V_{DD,i}^2) = \frac{E_i}{S_i} \end{array} \right.$ <p style="text-align: center;">energy constant linearly dependent</p> $\frac{\partial E / \frac{\partial D}{\partial S_i}}{\frac{\partial D}{\partial S_i}} = - \frac{E_i / S_i}{\tau_{nom} (h_i - h_{i-1})}$ <div style="border: 1px solid blue; padding: 5px; width: fit-content; margin: 10px auto;"> <math display="block">\frac{\partial E / \frac{\partial D}{\partial S_i}}{\frac{\partial D}{\partial S_i}} = - \frac{E_i}{\tau_{nom} (h_i - h_{i-1})}</math> </div>	<p style="text-align: center;">sensitivity of the energy delay curve</p> $D = \sum_i t d_i$ $t d_i = \frac{\partial t d_i}{\partial S_i}$ $\frac{\partial D}{\partial S_i} = \frac{\partial t d_i}{\partial S_i} + \frac{\partial t d_{i-1}}{\partial S_i}$ $= \tau_{nom} \frac{g_i}{\gamma} \frac{S_{i+1}}{S_i^2} + \tau_{nom} \frac{g_{i-1}}{\gamma} \frac{1}{S_{i-1}}$ $= - \tau_{nom} \left( \frac{g_i}{S_i} \frac{S_{i+1}}{\gamma} - \frac{g_{i-1}}{\gamma} \frac{S_i}{S_{i-1}} \right)$ $= - \frac{\tau_{nom}}{S_i} (h_i - h_{i-1}) \quad (\text{for } \gamma = 1)$
--	---

Figure 48: Sizing sensitivity

So the more a gate consumes, the more sensitive it is to sizing.

We can do the same thing for the sensitivity to the power supply:

$$\frac{\partial E / \frac{\partial D}{\partial V_{DD}}}{\frac{\partial D}{\partial V_{DD}}} \left| \begin{array}{l} E = \sum_i E_i \\ E_i = K_e S_i (V_{DD,i-1}^2 + \gamma V_{DD,i}^2) \\ = K_e S_i (1 + \gamma) V_{DD}^2 \\ \frac{\partial E}{\partial V_{DD}} = 2 K_e \left( \sum_i S_i \right) (1 + \gamma) V_{DD} = \frac{2 \cdot E}{V_{DD}} \end{array} \right.$$

Figure 49: Sensitivity PSS 1

Most sensitive to energy and fast gates. Maximal for  $V_{DD,max}$

## Example Chain of inverter

[!caution] I need to finish this bruh

$$\begin{aligned}
\left. \frac{\partial E / \frac{\partial V_{DD}}{\partial D}}{\frac{\partial D}{\partial V_{DD}}} \right| & \begin{array}{l} E = \sum_i E_i \\ \frac{\partial E}{\partial V_{DD}} = \frac{2 \cdot E}{V_{DD}} \end{array} \quad \left| \begin{array}{l} D = \sum_i t d_i \\ = \sum_i \left( \frac{K_d V_{DD}}{(V_{DD} - V_T)^\alpha} \left( 1 + \frac{1}{\gamma} \frac{S'_{i+1}}{S_i} \right) \right) \\ = K_d \frac{V_{DD}}{(V_{DD} - V_T)^\alpha} \sum_i \theta_i \\ \frac{\partial D}{\partial V_{DD}} = K_d \sum_i \theta_i \left( \frac{1}{(V_{DD} - V_T)^\alpha} - \frac{\alpha}{(V_{DD} - V_T)^{\alpha+1}} \right) \\ = K_d \sum_i \theta_i \frac{V_{DD}}{(V_{DD} - V_T)^\alpha} \left( \frac{1}{V_{DD}} - \frac{\alpha}{(V_{DD} - V_T)} \right) \\ = -D \left( \frac{-V_{DD} + V_T + \alpha V_{DD}}{V_{DD}(V_{DD} - V_T)} \right) \end{array}
\end{aligned}$$

Figure 50: Sensitivity PSS 2

$$\begin{aligned}
\left. \frac{\partial E / \frac{\partial V_{DD}}{\partial D}}{\frac{\partial D}{\partial V_{DD}}} \right| & \begin{array}{l} E = \sum_i E_i \\ \dots \\ \frac{\partial E}{\partial V_{DD}} = \frac{2 \cdot E}{V_{DD}} \end{array} \quad \left| \begin{array}{l} D = \sum_i t d_i \\ \dots \\ \frac{\partial D}{\partial V_{DD}} = -D \left( \frac{-V_{DD} + V_T + \alpha V_{DD}}{V_{DD}(V_{DD} - V_T)} \right) \end{array} \right. \\
\Downarrow & \quad \Downarrow \quad \Downarrow \\
\frac{\partial E / \frac{\partial V_{DD}}{\partial D}}{\frac{\partial D}{\partial V_{DD}}} &= \frac{E}{D} \frac{2V_{DD}(V_{DD} - V_T)}{V_{DD} + V_T + \alpha V_{DD}} \\
&= -\frac{E}{D} \frac{2V_{DD} \left( 1 - \frac{V_T}{V_{DD}} \right)}{V_{DD} \left( -1 + \frac{V_T}{V_{DD}} + \alpha \right)} \quad \Rightarrow \quad \boxed{\frac{\partial E / \frac{\partial V_{DD}}{\partial D}}{\frac{\partial D}{\partial V_{DD}}} = -\frac{E}{D} \frac{2 \left( 1 - \frac{V_T}{V_{DD}} \right)}{V_{DD} \left( \alpha - 1 + \frac{V_T}{V_{DD}} \right)}}
\end{aligned}$$

Figure 51: Sensitivity PSS 3

Minimize delay for given  $C_L$  and  $C_{in}=1$ ?

$$t = t_{p0} \cdot \left( 1 + \frac{C_{in2}}{C_{in1}} + 1 + \frac{C_{in3}}{C_{in2}} + \dots + 1 + \frac{C_L}{C_{inN}} \right)$$

$$\Rightarrow \min \left( \frac{S_2}{S_1} + \frac{S_3}{S_2} + \dots + \frac{F}{S_N} \right)$$


Each stage has the same effort  $f = C_{ext}/C_{in}$ , also called 'fixed taper'

$$\Rightarrow S_j = \sqrt{S_{j-1} S_{j+1}}$$

Each stage has the same delay

simple case without logical effort

Figure 52: Chain of inverter example

 

This is a variable taper instead of the constant taper for minimum delay

Figure 53: Effective fan-out



 


Figure 54: Change of PSS

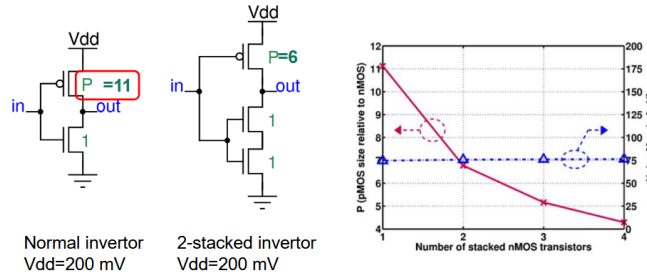


Figure 55: Low VDD inverter

## Ultra low voltage design examples

In this section, we will investigate some low voltage design:

It is a trade-off between the amount of stacking and the relative size and the noise margin. The more we stack the more sensitive it is to noise and a lil bleep could ruin the whole logical function.

This has been proven to help with the *variability*.

[!warning] Using this technique isn't ideal as the PMOS gets weak er and weaker, the excessive sizing of PMOS will result in higher area and capacitance !

This is where transmission gates really shine ! They are both on and they compensate each other. They take less area and they function in every corner and variability. Less leakage and good dynamic numbers.

But the NMOS in TG leaks too much and we have to increase this  $I_{on,p}/I_{off,n}$  ratio. Stacking will reduce  $I_{off,n}$  by a **factor 5**. Degrades the speed slightly.

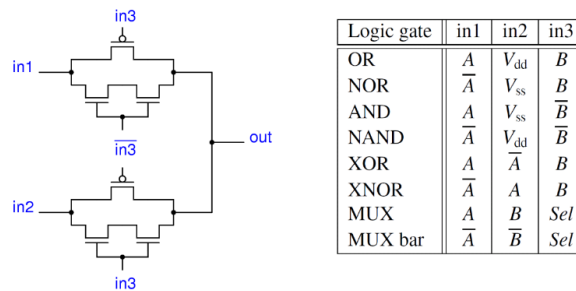


Figure 56: TG logic gate

- Good: low leakage, small area, low dynamic energy, 1 generic block, AND and OR possible
- Needs differential input, signal loss at output, lower speed, not well supported in modern library (need to create your own), delays go up **quadratically** with logic length.

**TG: Building pipelines**

We need to re-generate the logic with inverter and construct our own special library for this. We need some differential master-slave architecture. It is possible to build some RISC-V CPU in academic, but the industry doesn't really want this. On top of this, the gap between the driving strength of PMOS and NMOS is closing. Variability is worse and worse and we prefer simply redesigning for Ultra low VT application.